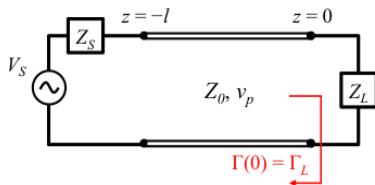


§ Impedance Matching Network.

3.1 Objective of Impedance Matching



Reflection Coefficient

$$T(z) = \frac{V^- e^{j\beta z}}{V^+ e^{-j\beta z}} = T_L e^{2j\beta z}$$

$$T_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$


Voltage Wave

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

$$I(z) = \frac{1}{Z_0} (V^+ e^{-j\beta z} - V^- e^{j\beta z})$$


When $Z_0 \neq Z_L \Rightarrow$ create reflected voltage wave $V^- e^{j\beta z}$.

$$\text{Wastes transmitting power } P_{av}(z) = \frac{|V|^2}{2Z_0} (1 - |T(z)|^2)$$

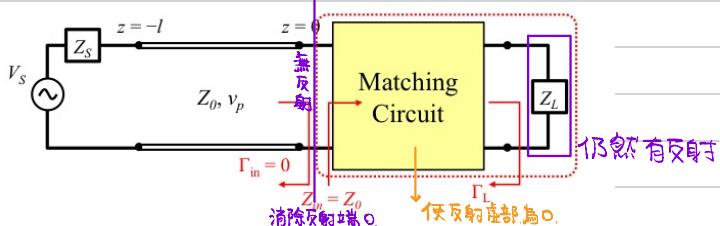

- with well design, making $Z_{in} = Z_0$ $|T_{in}| = 0$, no reflected voltage wave to source.

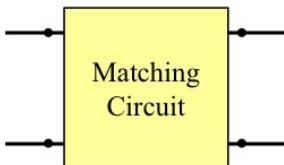- T_L exists matching circuits like buffer, storing transmitting power from V_s .



matching circuit must be lossless components.

- Lump Inductors, Capacitors

- Transmission-line stubs

Factors selecting matching circuit.

- complexity, 複雜度
- Implementation, 實作性

- Size 尺寸

- Bandwidth, 頻寬
- Adjustability, 可調性.

Technique of Impedance Matching.

Z_L is purely real:

quarter wavelength transformer.

Z_L is complex:


lump component.

single / double stubs.


Matching circuit for antenna applications:



Matching circuit for power amplifiers:

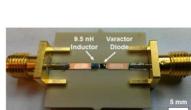

Power Delivered to Load.

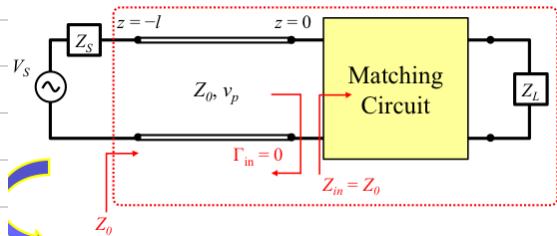

transmission line connects to match load.
⇒ impedance on any point Z is Z_0 .
not all power generated by source transmit to load.
to achieve maximum power. $Z_0 = Z_s^*$

Practical Scenario.


V_s, Z_s (assuming purely real). Z_L are given.

⇒ choose proper Z_0 , matching circuit that maximum power deliver to load.

choosing $Z_0 = Z_s$, design matching circuit that $Z_{in} = Z_s$.

power efficiency = 50% (maximum power to load)

3.2 Quarter Wavelength Transformers

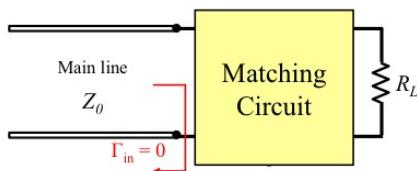


Z_0, R_L both real and given.

if $Z_0 \neq R_L$, (no matching network), then,

$$T_L = \frac{R_L - Z_0}{R_L + Z_0}$$

⇒ by using lossless piece of transmission line
of characteristic impedance Z_1 , length $\lambda_g/4$
where $Z_1 = \sqrt{Z_0 R_L}$

Theorem of quarter wavelength matching

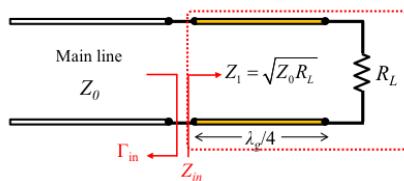


to having perfect matching, $\Rightarrow \Gamma_{in} = 0$

$$Z_{in} = Z_1 \left(\frac{R_L + j Z_1 \tan \beta l}{Z_1 - j R_L \tan \beta l} \right) \Rightarrow l = \frac{\lambda}{4} \quad \therefore Z_{in} = \frac{Z_1^2}{R_L}$$

if $Z_1 = \sqrt{Z_0 R_L}$ $Z_{in} = Z_0, T_{in} = 0$.

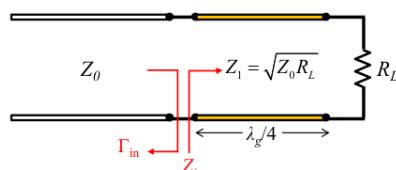Characteristics of $\lambda/4$ transformers



$\lambda/4$ transformers makes $T_{in} = 0$.

$Z_1 \neq R_L$: reflected wave still exists.
but all power successfully transmits to R_L .


* Drawbacks:

only when line length = $\lambda/4$,
perfect match only in one frequency.

limited to real-value load impedance



- $R_L = 100 \Omega$ and $Z_0 = 50 \Omega$ are given.
- Find the characteristic impedance of the matching section (Z_1)
- Plot $|T_{in}|$ vs. normalized frequency f/f_0 , where f_0 is the frequency at which the line is $\lambda/4$ long.

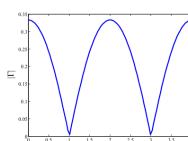

Frequency f	TL length l
$f = 0$	0
$f = 1f_0$	$l = \lambda_g/4$
$f = 2f_0$	$l = \lambda_g/2$
$f = 3f_0$	$l = 3\lambda_g/4$
$f = 4f_0$	$l = \lambda_g$

在 $f = f_0$ 與 $f = 3f_0$ 時,

$$\because \tan \beta l = \frac{\pi}{2}, \frac{3\pi}{2} \Rightarrow Z_1 = \sqrt{Z_0 R_L} \text{ (match)}$$

∴ 此時具有最小的 $|T_{in}|$.

characteristic impedance: $Z_1 = \sqrt{Z_0 R_L}$.


$Z_1 = 70.71 \Omega$.

$$|\Gamma_{in}| = \left| \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \right|$$

設計頻率的相切波長,

$$Z_{in} = Z_1 \frac{R_L + j \tan \beta l}{R_L - j \tan \beta l} \quad \beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda_0}{4} = \left(\frac{2\pi f}{f_0} \cdot \frac{\lambda_0}{4} \right) = \frac{\pi f}{2f_0}$$

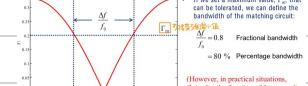- Therefore, the explicit formula is: $f/f_0 = \sqrt{\frac{Z_0 + Z_1}{Z_0 - Z_1}} \cdot \sqrt{\frac{Z_0 + Z_1}{Z_0 - Z_1} - 1}$
- If we set a maximum value, f_m , that can be tolerated, we can define the bandwidth of the matching circuit:



- For higher frequencies the line looks electrically longer
- For lower frequencies the line looks electrically shorter

→ 改變傳輸線長度 (偏移).


* The fractional bandwidth of a quarter-wavelength transformer can be derived as:


$$\frac{\Delta f}{f_0} = 2 \cdot \frac{4}{\pi} \cos^{-1} \left(\frac{\Gamma_{in}}{\sqrt{1 - \Gamma_{in}^2}} \frac{2\sqrt{Z_0 Z_1}}{|Z_1 - Z_0|} \right)$$

Γ_{in} Magnitude of the tolerable reflection coefficient

Z_1 Load impedance

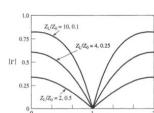Z_0 Characteristic impedance of the main line



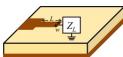

- Design a quarter-wavelength transformer to match $Z_L = 10 \Omega$ to $Z_0 = 50 \Omega$
- Design frequency: 1 GHz
- Requirement of tolerable bandwidth: VSWR < 1.5
- Materials at hand: FR4 substrate with $h = 1 \text{ mm}$ ($\epsilon_r = 4.4$)



- Find the length L .
- Find the width w .
- Find the characteristic impedance Z_0 .
- Find the operational bandwidth of this transformer.

$$Z_1 = \sqrt{Z_0 Z_L} = 22.36 \Omega \quad \text{at } VSWR = 1.5.$$

$$\text{freq} = 1 \text{ GHz} \Rightarrow \lambda = 0.3 \text{ m.}$$

$$T_m = \frac{1.5 - 1}{1.5 + 1} = 0.2.$$

$$W = 6.03 \text{ mm.}$$


$$\frac{\Delta f}{f_0} = 29\%.$$

$$E_{eff} = 3.71.$$

$$\lambda_{\frac{1}{2}} = \frac{\lambda_0}{\sqrt{E_{eff}}} = 155.7 \text{ mm.}$$

$$L = \frac{\lambda_{\frac{1}{2}}}{4} = 38.94 \text{ mm.}$$

3.3 Matching with Lump Elements

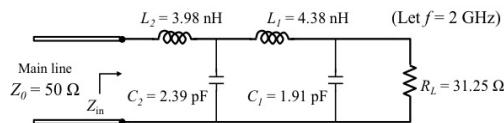

	L	C
Impedance	$j\omega L$	$-j\frac{1}{\omega C}$
Nor. Impedance	$j\omega L$	$-j\frac{1}{\omega C Z_0}$
Admittance	$-j\frac{1}{\omega L}$	$j\omega C$
Nor. Admittance	$-j\frac{1}{\omega L Y_0}$	$j\omega C$

Series 跨接.

Shunt 跨接.

For series connection.


Using Z chart

Impedance moves constant Γ circle

For shunt connection.

Using Y chart

Admittance moves constant Γ circle

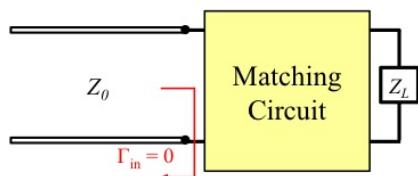

if $Z_0 \neq Z_L$


$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad (\text{mismatch})$$

by applying matching circuit

designing combination reactive elements < L型>

reactive components be inductors or capacitors


L-section: Using 2 reactive elements

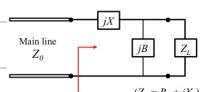

- Goal: $Z_m = Z_0$ (so that $\Gamma_m = 0$)
- Used for $R_L > Z_0$
- Analytic solutions (2 solutions):

$$X_L = \frac{R_L(R_L^2 + X_L^2 - Z_0^2)}{Z_0^2 + X_L^2}$$
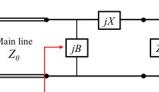
$$X_L = \frac{1}{B} + \frac{X_L Z_0}{R_L} - \frac{Z_0}{B R_L}$$



- Goal: $Y_m = Y_0$ (so that $\Gamma_m = 0$)
- Used for $R_L < Z_0$
- Analytic solutions (2 solutions):

$$X_L = \pm \sqrt{R_L(Z_0 - R_L)} - X_L$$

$$B = \frac{X_L + X_0}{Z_0 R_L}$$

1. $R_L < Z_0$

在匹配时往往第二步要回到 $\Gamma.g=1$ circles

若 $R_L < Z_0$. 同理联供 R_L 变大回到 $\Gamma.g=1$ circles.

⇒ 先集角差.



2. $R_L > Z_0$

同理要使 R_L 回到 $\Gamma.g=1$ circles

用集供 R_L 变小回到 $\Gamma.g=1$ circles.

⇒ 先集角差.


Dynamic Range (white area)

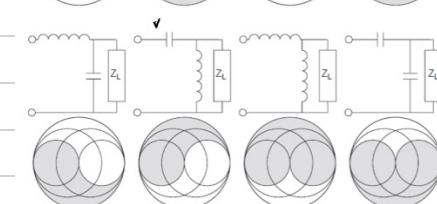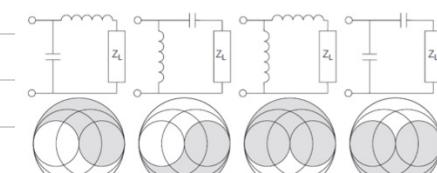

Characteristic of L-shape circuit

- Lump elements have smaller size
 - Lump elements better adjustability
 - provide wider bandwidth.
- ⇒ may not be realizable at high frequency.
- ⇒ inductance, capacitance discrete. chosen over limited ranges values


Real-World Capacitors

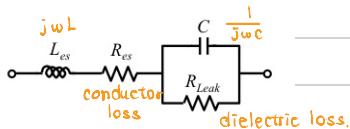


R_{cs} : 平行金属板电容的连接.

L_{cs} : 随频率↑其等效电路容值↓,造成感值为主导.

R_{leak} : 介电质损耗.

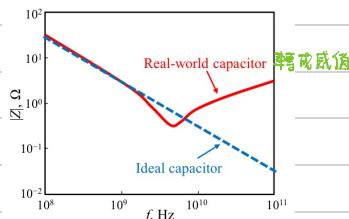


Real-World Inductors

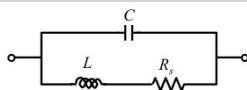

R_s : 线圈损耗.

C : 电感线圈间线匝容值.

Frequency response in log scale:

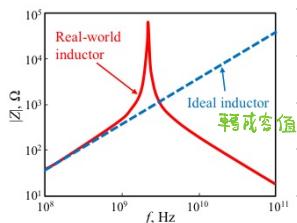


随频率↑其等效电路并联感值↓,并联容值↑.

3.4 Matching with TL stubs

$$\text{由 } Z_{th} = Z_0 \cdot jZ_0 \tan \beta z, \\ Z_{th} = jZ_0 \tan \beta z.$$

$$\Rightarrow Z_L = 0 \text{ 時}, Z_{th} = -jZ_0 \tan \beta z. \quad (\text{電容})$$
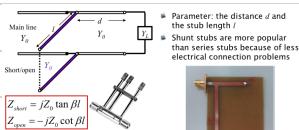
$$Z_L = \infty \text{ 時}, Z_{th} = jZ_0 \cot \beta z. \quad (\text{電感}).$$



$$Z_{short} = jZ_0 \tan \beta l \\ Z_{open} = -jZ_0 \cot \beta l$$

- For stubs using coaxial cable:
short-circuited stubs are more popular than the open-circuited stubs because of less radiation

- For stubs using microstrip lines:
open-circuited stubs are easier to fabricate than the short-circuited stubs

Problem statement:

1. (3 pts) A load impedance $Z_L = 30 - j40 \Omega$ is to be matched to a 50Ω transmission line using a single series stub tuner. Find two solutions (d_1, l_1, d_2 and l_2) using open-circuited stubs by the Smith chart.

CX.



- For a load impedance $Z_L = 30 - j40 \Omega$, design a single-shunt stub tuner to match it to a 50Ω transmission line. The operating frequency is $2 GHz$.
- For each solution, calculate the reflection coefficient magnitude from $1 GHz$ to $2 GHz$ for each solution.



$$1. Z_L = 50, Z_0 = 50-j50, f = 2GHz, \\ Z_m = 1 + j1.6$$

1. 並聯短路
看點: $0.217\lambda - 0.317\lambda = 0.11\lambda$,
此時 Z -chart $1-j1.44$
 \rightarrow 用 $-j1.44$ 消除 0.09λ
看點: $(0.0705 + 0.217)\lambda = 0.266\lambda$,
此時 Z -chart $1-j1.44$,
 \rightarrow 用 $-j1.44$ 消除 0.09λ

2. 並聯開路
看點: $0.217\lambda + 0.317\lambda = 0.534\lambda$,
此時 Z -chart $1+j1.44$
 \rightarrow 用 $-j1.44$ 消除 0.09λ
看點: $(0.0705 - 0.217)\lambda = 0.266\lambda$,
此時 Z -chart $1+j1.44$

3. 短聯開路
看點: $0.324\lambda + 0.3151\lambda = 0.639\lambda$,
此時 Z -chart $1+j1.5$,
 \rightarrow 用 $-j1.5$ 消除 $0.156\lambda - 0.5\lambda = 0.406\lambda$,
看點: $(0.0705 - 0.324\lambda) = 0.216\lambda$,
 \rightarrow 用 $-j1.5$ 消除 $0.0705 - 0.315\lambda = 0.36\lambda$

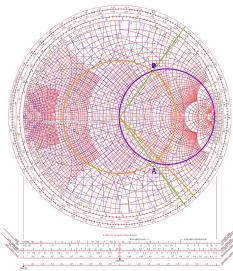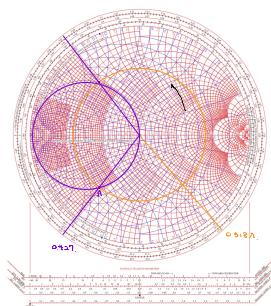4. 短聯短路
看 A 點: 0.09λ ,
 \rightarrow 用 $-j1.5$ 消除 $0.156\lambda - 0.5\lambda = 0.406\lambda$,
看 B 點: 0.36λ ,
 \rightarrow 用 $-j1.5$ 消除 $0.406\lambda - 0.36\lambda = 0.15\lambda$



Characteristic of Matching Single Stubs.

• 對於任意頻率皆可使用。

• 闊易製作。

• 可用於高頻。

⇒ Limitation.

• 大尺寸。

• 靈活度低。

Matching with double