

2.2 Frequency-Domain Analysis.

• Getting Complete Signal Expression.

$$\tilde{V}(z, t) = V^i(t - \frac{z}{v_p}) + V^r(t + \frac{z}{v_p})$$

Voltage source $\Rightarrow V^i, V^r$ related to source impedance, load impedance, voltage source.
⇒ by using sinusoidal wave, we can have phasor expression.

$$\tilde{V}_s(z, t) = A \cos[\omega(t - \frac{z}{v_p}) + \phi]$$

Amplitude \downarrow angular frequency $\omega = 2\pi f$.

from definition of phase velocity, $v_p = \frac{\Delta z}{\Delta t} = \frac{\lambda}{T} = \lambda f = \left(\frac{\lambda}{2\pi}\right) \cdot \left(2\pi f\right)$

$$\therefore v_p = \lambda f = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$

apply in phasor transform $V(z) = V e^{-j\beta z + \phi}$.

$$\text{apply telegraph equation in frequency domain.} \Rightarrow \begin{cases} \frac{\partial V(z, t)}{\partial z} = -L \frac{\partial I(z, t)}{\partial t} \\ \frac{\partial I(z, t)}{\partial z} = -C \frac{\partial V(z, t)}{\partial t} \end{cases} = \begin{cases} \frac{dV(z)}{dz} = -j\omega L I(z) \\ \frac{dI(z)}{dz} = -j\omega C V(z). \end{cases}$$

在頻域 (phasor domain) 並無時間關係。

$$\frac{d^2V}{dz^2} = -j\omega L \frac{dI}{dz} \leftarrow \text{代入.} \quad \frac{d^2V}{dz^2} = -\omega^2 LC V \Rightarrow \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} \quad \beta = \omega \sqrt{LC}$$

$$V(z) = V^i e^{j\beta z} + V^r e^{j\beta z}, \text{ and } I \text{ is vice versa.}$$

inverse phasor transform $\rightarrow V^i = \text{Re}\{V(z)\} = \frac{V^+(z) + V^-(z)}{2}$


knowing, V^+ means incident wave, V^- means reflect wave.

$$-\frac{z}{v_p}$$


$$\Rightarrow \text{define "reflection coefficient"} T(z) = \frac{V^- e^{j\beta z}}{V^+ e^{j\beta z}} = \left(\frac{V^-}{V^+}\right) e^{j\beta z}. \quad <\text{special case at } z=0, T(0) = \frac{V^-}{V^+}$$

$$V(z) = V^+ e^{j\beta z} + V^- e^{j\beta z} = V^+ e^{j\beta z} (1 + T(z)) \quad \Rightarrow \text{input impedance } Z(z) = \frac{V(z)}{I(z)} = Z_0 \frac{1 + T(z)}{1 - T(z)}$$
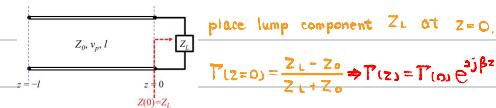
$$\text{transfer to. } \frac{Z(z)}{Z_0} = \frac{1 + T(z)}{1 - T(z)} \Rightarrow (Z(z) + Z_0) T(z) = Z(z) - Z_0 \Rightarrow T(z) = \frac{Z(z) - Z_0}{Z(z) + Z_0}.$$



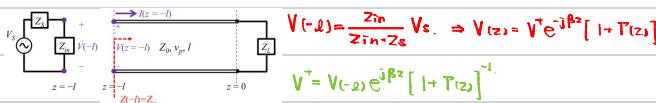
$$T(z=0) = \frac{Z_L - Z_0}{Z_L + Z_0} \Rightarrow T(z) = T(0) e^{j\beta z} < T(0) = T_L >$$



$$\text{Apply all the coefficient } V(z) = V_s \frac{1}{1 + T(z)} \frac{Z_0}{Z_0 + Z_L} e^{-j\beta z} (1 + T(z))$$

• Impedance Transformation.

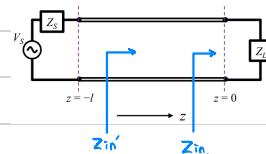

$$\begin{aligned}
 Z(z) &= Z_0 \frac{1+T(z)}{1-T(z)} \\
 &= Z_0 \frac{1 + \frac{Z_L - Z_o}{Z_L + Z_o} e^{2j\beta z}}{1 - \frac{Z_L - Z_o}{Z_L + Z_o} e^{2j\beta z}} = Z_0 \frac{(Z_L + Z_o)(\cos\beta z - j\sin\beta z) + (Z_L - Z_o)(\cos\beta z + j\sin\beta z)}{(Z_L + Z_o)(\cos\beta z - j\sin\beta z) - (Z_L - Z_o)(\cos\beta z + j\sin\beta z)} \\
 &= Z_0 \frac{\frac{Z_L + Z_o}{2} e^{j2\beta z} + \frac{Z_L - Z_o}{2} e^{-j2\beta z}}{\frac{Z_L + Z_o}{2} e^{j2\beta z} - \frac{Z_L - Z_o}{2} e^{-j2\beta z}} = Z_0 \frac{Z_L + jZ_o \tan\beta z}{Z_L - jZ_o \tan\beta z}
 \end{aligned}$$

- Average Power along Lossless TL.

若為 rms phasor 則不須乘 $\frac{1}{2}$

$$\text{Power} = \frac{1}{2} \operatorname{Re}\{V(z_2) I(z_2)^*\}$$

$\hat{\zeta} T(z_2) = U + jV$

$$= \frac{1}{2} \operatorname{Re}\left\{ V^* e^{jBz} \left[|+T(z_2)| \frac{V e^{jBz}}{Z_0} \left[|+T(z_2)|^* \right] \right] \right\}$$

$$\begin{aligned} (+T(z_2)) (|+T(z_2)|^*) &= (|+U|) - j(|+U)V^* - V^2 \\ &= (|+U|) - j2V - V^2 \end{aligned}$$

$$= \frac{|V|^2}{2Z_0} \operatorname{Re}\left\{ (|+U| - j2V - V^2) \right\} = \frac{|V|^2}{2Z_0} \left[|+U| - j2V - V^2 \right]$$

reflect power

• Return Loss & Insertion Loss.

Return Loss

→ power reflect.

$$RL = -10 \log \left(\frac{P_o}{P_i} \right)$$

↓ power transmit to load.

$$= -10 \log \left(\frac{|V_o|}{|V_i|} \right)^2 = -20 \log |T(z)| = -20 \log |T_L|$$

$$= \frac{V_1^2}{2Z_0} [1 - |P(z_1)|^2]$$

Insertion Loss

$$IL = -10 \log \left(\frac{P^t}{P_i} \right) = -10 \log \left(\frac{P^t - P^f}{P_i} \right) = -10 \log \left(1 - \frac{P^f}{P^t} \right)$$

• Special Case of Input Impedance

1. $Z_L = 0$. <short>

$$RL = -20 \log |T_L| = -20 \log \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right| = 0 \text{dB.}$$

$$2. Z_1 = \infty \quad <\text{open}>$$

$$RL = -20 \log |T_L| = -20 \log \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right| = 0 \text{ dB.}$$

$$3. Z_L = Z_0 \longrightarrow Z(z) = Z_0 \frac{1 + T(z)}{1 - T(z)} = Z_0, (T'(z) = T_z e^{\frac{2j\pi f z}{\lambda}} = 0)$$

$$R_L = -20 \log |P_L| = 0 \text{ 平方米} \rightarrow \text{完全反射输出}$$

$$4. \quad Z = \frac{\lambda}{2} \longrightarrow Z_{(Z)} = Z_0 \frac{Z_L - Z_0 \tan \beta Z}{Z - Z_0 + j Z_0 \tan \beta Z} = Z_L, \quad (\tan \beta Z = \tan \frac{2\pi}{\lambda} \cdot \frac{\lambda}{2} = 0)$$

$$5. \quad Z = \frac{\lambda}{4} \longrightarrow Z(z) = Z_0 \frac{Z_L - Z_0 \tan \beta z}{Z_L + Z_0 \tan \beta z} = \frac{Z_0^2}{Z_0^2 + \tan^2 \beta z} \quad (\tan \beta z = \tan \frac{\pi z}{\lambda}, \frac{\lambda}{4} = \infty)$$

• Voltage Standing Wave Ratio

1. Voltage Standing Wave Phenomenon.

$$\text{from } V(z) = V^* e^{-j\beta z} + V e^{j\beta z} = V e^{-j\beta z} [1 + \Gamma(z)] = V e^{-j\beta z} [1 + \frac{Z_L - Z_0}{Z_L + Z_0} e^{j\beta z}]$$

at short circuit $\Gamma_L = 0$. $V(z) = V^* e^{-j\beta z} [1 - e^{j\beta z}]$ having perfect standing wave because of $V_{min}=0$.

open circuit $\Gamma_L = \infty$ $V(z) = V^* e^{-j\beta z} [1 + e^{j\beta z}]$ having perfect standing wave because of $V_{max}=0$.

Conclusion: only have perfect standing wave when $1 + \Gamma(z) = 0$ for particular z .
and else there having similar phenomenon.

2. Extreme Value of $V(z)$.

from conclusion above, we can knew when extreme value exists, then.

$$|V_{max}| = |V^*| (1 + |\Gamma_L|)$$

$$|V_{min}| = |V^*| (1 - |\Gamma_L|)$$

3. Voltage Standing Wave Ratio.

to define measure of "mismatching line" define VSWR.

$$\text{VSWR} = \frac{|V(z)|_{\max}}{|V(z)|_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$


for matching load: VSWR=1,
for open or short: VSWR= ∞

4. Some Useful Number

$\text{VSWR} = 2:1$	VSWR	$ T(z) $	R.L.	$1 - T(z) ^2$
10 dB threshold	50%	3dB	50%	
$\text{VSWR} = 3:1$	3.73%	6dB	75%	
6 dB threshold.	3.16%	7dB	80%	
$\text{VSWR} = 1.5:1$	20%	7dB	80%	
14 dB threshold. $z \approx 1.96$	10%	10dB	90%	
$\text{VSWR} = 2.5:1$	5%	13dB	95%	
17.4 dB threshold.	1%	20dB	99%	


2.8 Smith Chart

Properties of T plane and Z plane

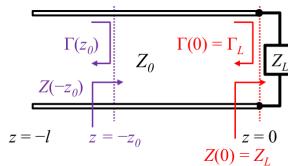

from $Z(z) = Z_0 \frac{Z_L + jZ_0 \tan \beta z}{Z_0 - jZ_L \tan \beta z}$ → $Z(z)$ 阻抗會隨位置不同而改變大小。
⇒ 說明負負載可依循。


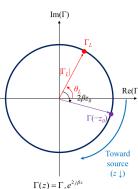
from $T(z) = \Gamma_L e^{2j\beta z}$ → 在定 Z_0 的狀況下, 其反射係數僅跟位置有關。
⇒ 大小固定, 僅需反射參數變換。
可用 T plane 來實行



T plane to make impedance



Slotted Line Measurements.

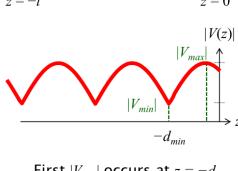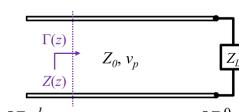

1. 在 $-d_{min}$ 時有最小的 Γ .

$$\Gamma(z_1) = \Gamma_L e^{2j\beta z_1}$$

$$= \Gamma_L e^{2j\frac{\lambda}{\lambda}(-d_{min})} = -\Gamma_L$$


$$\therefore d_{min} = \frac{\lambda}{4}$$

$$2. \text{VSWR} = \frac{1 + |\Gamma|}{1 - |\Gamma|} \Rightarrow |\Gamma| = \frac{\text{VSWR}-1}{\text{VSWR}+1}$$

$$3. \text{最後, } Z_L = Z_0 \frac{1 - \Gamma_L}{1 + \Gamma_L}$$

First $|V_{min}|$ occurs at $z = -d_{min}$

Concept of Smith Chart

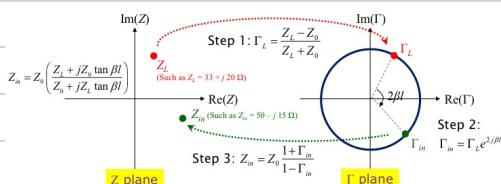

$\because \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$ 會有 Z_0 不知量 ⇒ 會進行標準化

才可讓 Γ 不會受到 Z_0 的影響 ⇒ $Z_0 = \frac{Z_L}{\Gamma_L}$.

Step 2:

$\Gamma_{in} = \Gamma_L e^{2j\beta l}$

Normalized Impedance on Γ Plane

由上式可知, $Z_n = \frac{1+\Gamma}{1-\Gamma}$, 令 $Z_n = \Gamma + jX$, $\Gamma = u + jv$.

$$\therefore \Gamma + jX = \frac{1+\Gamma}{1-\Gamma} = \frac{1+u+jv}{1-u-jv} = \frac{(1+u+jv)(1-u+jv)}{(1-u-jv)(1-u+jv)} = \frac{1-u^2-v^2+j2v}{(1-u)^2+v^2}$$

$$\text{得出 } \Gamma = \frac{1-u^2-v^2}{(1-u)^2+v^2}, \quad X = \frac{2v}{(1-u)^2+v^2}$$

1. 求 Γ 的关系:

$$r(1-u^2+v^2) = 1-u^2-v^2$$

$$(1+r)v^2 = (1-r) + 2uv - (1+r)u^2$$

$$v^2 = \frac{1-r}{1+r} + \frac{2uv}{1+r} - u^2$$

$$v^2 = \frac{1-r^2}{(1+r)^2} + \frac{2uv}{1+r} - u^2$$


$$(\frac{1}{r+1})^2 = (u - \frac{r}{r+1})^2 + v^2$$

2. 求 X 的关系:


$$(1-u)^2 + v^2 = \frac{2v}{X}$$

$$(1-u)^2 + (v - \frac{2v}{X} + \frac{1}{X^2}) = \frac{1}{X^2}$$
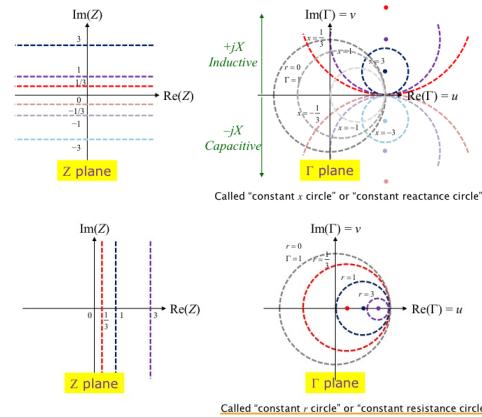
$$(1-u)^2 + (v - \frac{1}{X})^2 = (\frac{1}{X})^2$$



Basic Procedure of Smith Chart

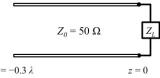

* A load impedance of $130 + j90 \Omega$ terminates a 50Ω transmission line that is 0.3 λ long.

- 1. Find the reflection coefficient at the load
- 2. Find the reflection coefficient at the input to the line
- 3. Find the VSWR on the line
- 4. Find the return loss
- 5. Find the impedance seen at the input to the line
- 6. Find the admittance seen at the input to the line

1. 先正規化 $Z_n = \frac{Z_L}{Z_0}$, 並找共軸 Γ 圖

2. 將 Γ 圖交點列出並以圓點為圓心找出支點長度.

3. 將長度與外圓的半徑做比例比較, 即得 r .

4. 芒哥找 $Z(z)$ 可直接用 Smith Chart 繪圖, 以 $\frac{\pi}{2}$ 分之 Z 繪.

Connecting Z_L with Series.

1. Inductor:

$\because Z = j\omega L \Rightarrow \therefore$ 對於 $Z_n = \Gamma + jX$ 來說, 其 "X" 的成份變大. → 見察某頻率可知 f 大會往 x 大方向走.

其結果為定 Γ 圖, 朝 x 大方向走.

若又看頻率某頻率不會使 x 從正到負, 負到正.

2. Capacitor:

$\because Z = -j\frac{1}{\omega C} \Rightarrow \therefore$ 對於 $Z_n = \Gamma + jX$ 來說, 其 "X" 的成份變小. → 見察某頻率可知 f 大會往 x 小方向走.

其結果為定 Γ 圖, 朝 x 小方向走.

3. Resistor:

串聯電阻會使 $Z_n = \Gamma + jX$ 變大. → 見頻率無關.
其結果為定 Γ 圖朝 x 大方向走.





• Connecting Z_L with Parallel.

⇒ If we using parallel, the impedance would be complicated because of $Z_{in} = \frac{Z_1 Z_2}{Z_1 + Z_2}$


↳ changing to "admittance" form then $Y_{in} = Y_1 + Y_2 \Rightarrow$ methods to change Z_m to Y_m is $Z(\frac{\lambda}{4}) = Z_0 \frac{Z_0}{Z_L}$

$$\Rightarrow \frac{Z_L}{Z_0} = \frac{Z_0}{Z(\frac{\lambda}{4})} \text{ gets } Z_r|_{z=\frac{\lambda}{4}} = Y_L \text{ 實際上為將 } Z_L \text{ 旋轉 } 180^\circ$$

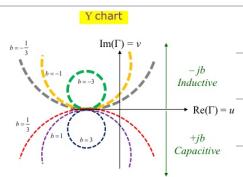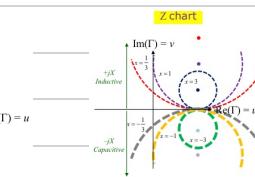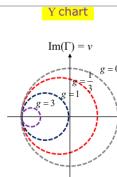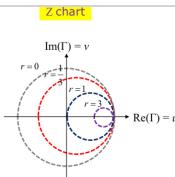another approach to get is rotating axis in 180°



2.4 Lossy Transmission Lines

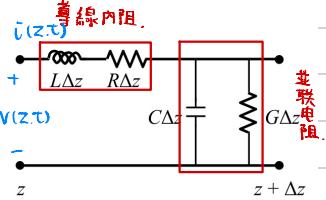

Why does loss exist

R: imperfect conductors (非良導體)

理想狀況下, $\sigma \rightarrow \infty$ 為導體而言其導電率 $\sigma = \infty$ (γ_m)

目前狀況, 石墨烯最佳.

G: imperfect dielectric (非良絕緣體)

理想狀況下, $\epsilon \rightarrow 0$.

R.G. distributed element ($\Delta z/m$)

at low frequency, $Z_L = j\omega L \rightarrow 0$.

$$Y_C = j\omega C \rightarrow 0.$$

$$G(\omega) \propto \sigma(\omega), \text{ and } \sigma(\omega) \propto \omega \rightarrow 0.$$

Revise KVL. dielectric conductivity.

$$-\nabla V(z,t) + (L\Delta z) \frac{\partial i(z,t)}{\partial t} + (R\Delta z) i(z,t) + \gamma(z+\Delta z, t) = 0.$$

$$\Rightarrow \text{phasor expression } \frac{dV}{dz} = -[R+j\omega L].$$

Revise KCL

$$-i(z,t) + (C\Delta z) \frac{\partial v(z+\Delta z, t)}{\partial t} + (G\Delta z)v(z+\Delta z, t) + i(z+\Delta z, t) = 0$$

$$\Rightarrow \text{phasor expression } \frac{di}{dz} = -(G-j\omega C)V$$

$$\Rightarrow \text{getting } \frac{d^2V}{dz^2} - k^2 V = 0. \quad V = \sqrt{(R+j\omega L)(G+j\omega C)} = \alpha + j\beta.$$

case 1: Lossless.

$$V = \sqrt{(R+j\omega L)(G+j\omega C)} = j\omega \sqrt{LC} \Rightarrow \alpha = 0, \beta = \omega \sqrt{LC}$$

case 2: Low loss, high frequency. ($R \ll \omega L, G \ll \omega C$)


$$V = \sqrt{(R+j\omega L)(G+j\omega C)} = \sqrt{\left(\frac{R}{j\omega L} + 1\right)\left(\frac{G}{j\omega C} + 1\right)} (\sqrt{j\omega L \times j\omega C})$$

= 2項式展開.

$$\approx j\omega \sqrt{LC} \sqrt{1 + \frac{R}{j\omega L} + \frac{G}{j\omega C}} \approx j\omega \sqrt{LC} \left[1 + \frac{1}{2} \left(\frac{R}{j\omega L} + \frac{G}{j\omega C} \right) \right]$$

$$\Rightarrow \text{getting } \alpha = \frac{1}{2} \frac{R}{j\omega L} + \frac{1}{2} \frac{G}{j\omega C}, \quad \beta = \omega \sqrt{LC}, \quad Z_0 = \sqrt{\frac{L}{C}}$$

conductor loss
dielectric loss.

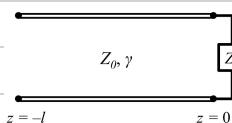

In time domain expression.

$$V(z,t) = \operatorname{Re}\{V(z)e^{j\omega t}\}$$

$$= |V|^2 e^{j\omega t} \cos(\omega t - \beta z + \phi) + |V|^2 e^{-j\omega t} \cos(\omega t + \beta z + \phi)$$

Incident Wave

Reflect Wave

* two waves contains an attenuation of coefficient $e^{-\alpha z}$.

Comparison

Lossless lines	Lossy lines
$\beta = \omega \sqrt{LC}$	$\gamma = \alpha + j\beta$
$Z_{in} = Z_0 \left(\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right)$	$Z_{in} = Z_0 \left(\frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l} \right)$
$P_{av}(z) = \frac{ V ^2}{2Z_0} (1 - \Gamma(z) ^2)$	$P_{av}(z) = \frac{ V ^2}{2Z_0} (1 - \Gamma(z) ^2) e^{-2\alpha z}$


→ 路長度有不同長度的旋轉與縮減

→ 有-丁 $e^{-2\alpha z}$ 縮減波

Attenuation of line (insertion loss) = $-10 \log e^{-2\alpha l} = d \ell \times 8.69 \text{ dB.}$

Three-Dimensional Structures

Parallel-plate waveguide

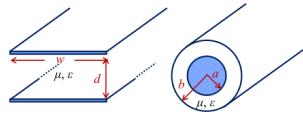


$$\epsilon = \epsilon' - j\epsilon'' = \epsilon'(1 - j\tan\delta) = \epsilon' + j(\sigma/\omega)$$

Coaxial cable



Parallel cylindrical wires

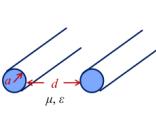

$$\epsilon = \epsilon' - j\epsilon'' = \epsilon'(1 - j\tan\delta) = \epsilon' + j(\sigma/\omega)$$

ϵ' (能量集中), ϵ'' (能量外扩)

$$\epsilon = \epsilon'(1 - j\tan\delta)$$

$$\text{loss tangent } \tan\delta = \frac{\sigma}{\omega\epsilon}$$

$$C = \epsilon' \frac{w}{d}$$

$$C = \frac{2\pi\epsilon'}{\ln(b/a)}$$

$$C = \frac{\pi\epsilon'}{\cosh^{-1}(d/2a)}$$

$$L = \mu \frac{d}{w}$$

$$L = \frac{\mu}{2\pi} \ln \frac{b}{a}$$

$$L = \frac{\mu}{\pi} \cosh^{-1}(d/2a)$$

$$Z_0 \approx \sqrt{\frac{L}{C}} = \sqrt{\frac{\mu}{\epsilon'} \frac{d}{w}}$$

$$Z_0 \approx \sqrt{\frac{L}{C}} = \frac{1}{2\pi} \sqrt{\frac{\mu}{\epsilon'}} \ln \frac{b}{a}$$

$$Z_0 \approx \sqrt{\frac{L}{C}} = \frac{1}{\pi} \sqrt{\frac{\mu}{\epsilon'}} \cosh^{-1}(d/2a)$$

$$R = \frac{2R_s}{w}$$

$$R = \frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right)$$

$$R = \frac{R_s}{\pi a}$$

$$G = \omega \epsilon' \frac{w}{d}$$

$$G = \omega \epsilon'' \frac{2\pi}{\ln \frac{b}{a}}$$

$$G = \omega \epsilon'' \frac{\pi}{\cosh^{-1}(d/2a)}$$

$$R_s \text{ (surface resistance)} = \frac{1}{\sigma \epsilon_s} \quad \delta_s = \sqrt{\frac{2}{\omega \mu \sigma}}$$

$$R_s = \frac{1}{\sigma \epsilon_s}$$

肌肤深动，电场一般仅通过表面

但不可能有理想导体 电流会进入到里面
造成肌肤深动。

G在频率较高时必须考虑。

EM Properties in some Dielectrics.

$$\text{Phase Velocity } V_p = \sqrt{\frac{1}{\epsilon \mu}} = \sqrt{\frac{1}{\epsilon_0 \epsilon_r \mu_0}} = \frac{C}{\sqrt{\epsilon_r}}$$

$$\Rightarrow \text{wavelength in material. } \lambda_d = \frac{V_p}{f} = \frac{\lambda_0}{\sqrt{\epsilon_r}}$$


the larger dielectric constant: smaller associated wavelength.

Material	Dielectric constant (ϵ_r)
Air	1.0054
FR4 (玻璃纖維板)	4.4
Epoxy (環氧樹脂)	3.9
Polyimide (聚亞醯胺)	4.5
Polytetrafluoroethylene (聚四氟乙烯)	2.1

Material	Dielectric constant (ϵ_r)
Polystyrene (聚苯乙烯)	2.5 - 2.6
Polypropylene (聚丙烯)	2.25
Ceramic (陶瓷)	3 - 7
Duroid RO 5880	2.2
Duroid RO 4003	3.55

Practical Issues of 3-D TLs

Parallel cylindrical wires:

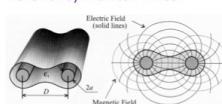

- A bad example of transmitting RF voltage and current waves

- Electric and magnetic field lines emanating from the conductors extend to infinity and thus tend to influence electronic equipment in the vicinity of the lines

- Radiation loss tends to be very high


- Applications: connecting TV set to receiving antenna, 50-60 Hz power line, and local telephone connection

- Used for almost all cases of RF systems or measurement equipment (up to 18 GHz)

- The outer conductor is grounded, so the radiation loss and field interference are minimized

- Coaxial connectors: a special structure of coaxial cable

Coaxial cable:

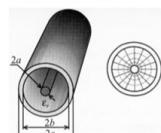


(特征阻抗跟内外半径有关)

RG or M17	Characteristic impedance (Ω)	Dielectric Type	Loss at 1 GHz (dB/100 ft)	Capacitance (pF/ft)
RG 8A/U	50	PE	9.0	29.5
RG 213A/U	50	Foam PE	9.0	30.8
RG 188A/U	50	Solid TFE	30.0	29.4
RG 179B/U	75	Solid TFE	25.0	19.5
RG 141A/U	50	Solid TFE	13.0	29.4
M17/90	93	Air space PE		13.5
M17/56	95	PE		17.0
M17/6	75	PE		20.6
M17/95	95	Solid TFE		15.4


Coaxial Cable Data Sheet

Reasons for using 50- Ω Coaxial Lines

For the aspect of loss:

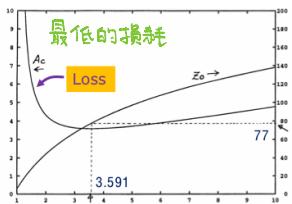

For the aspect of breakdown:

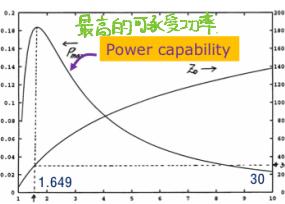


- Different geometric parameters result in different Z_0 and different α
- For an air-filled coaxial line, loss has the minimum value at $Z_0 = 77 \Omega$

- Different geometric parameters result in different power capacity (that is, the time-average power at breakdown)
- For an air-filled coaxial line, power capability has the maximum value at $Z_0 = 30 \Omega$

→ To compromise between 77Ω and 30Ω , we choose $Z_0 = 50 \Omega$

- Type-N connector:** The outer diameter of the female end is 0.625 in. (passband: 11-18 GHz)
- TNC connector:** This connector is similar to the very common BNC connector (passband: up to 1 GHz)
- APC-7 connector:** This connector is sexless (passband: up to 18 GHz)
- SMA connector:** The outer dimension of the female end is 0.25 in. This connector can be used up to 18-25 GHz and is the most popular coaxial connector for RF and microwave measurement applications

Planar Structures.

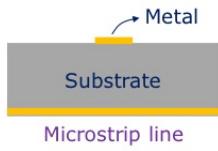

Coplanar waveguide (CPW)

Coplanar strip (CPS)

good for microwave integrated circuit applications


⇒ problem of Field Leakage.

PCB transmission line:

- They have rather high radiation loss (in comparison with 3-D TLs)
- They are prone to "crosstalk" (interfere) between neighboring conductor systems
- The severity of field leakage depends on the relative dielectric constants
- Substrates having high dielectric constants can minimize field leakage and cross coupling

- Z_0 , α , β depend on geometric characteristics dielectric properties ϵ_r .
- carefully determined geometric characteristics a number Z_0 is obtained.

Microstrip Lines

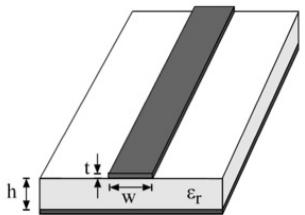


EM characteristics in MSL

$$\text{phase velocity in MSL: } V_p = \frac{C}{\sqrt{\rho_{eff}}}$$

$$\text{wavelength in MSL: } \lambda = \frac{\omega_p}{f} = \frac{\lambda_0}{\sqrt{\epsilon_{eff}}}$$


- Effective dielectric constant: the dielectric constant of a homogeneous medium that replaces the air and dielectric regions
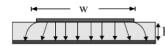
$$\mathcal{E}_{\text{eff}} = \mathcal{E}_r$$



- For very narrow lines ($w/h \ll 1$)
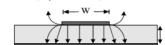
$$\mathcal{E}_{\text{eff}} = \frac{\mathcal{E}_r +}{2}$$




Analysis:

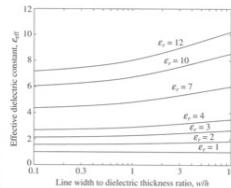1. If the line width is narrow ($w/h \leq 1$)

$$Z_0 = \frac{60}{\sqrt{\varepsilon_{eff}}} \ln \left(8 \frac{h}{w} + \frac{w}{4h} \right)$$


$$\text{where } \varepsilon_{\text{eff}} = \frac{\varepsilon_r + 1}{2} + \frac{\varepsilon_r - 1}{2} \left[\left(1 + 12 \frac{h}{w} \right)^{-0.5} + 0.04 \left(1 - \frac{w}{h} \right)^2 \right]$$



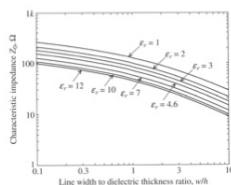2. If the line width is wide ($w/h \geq 1$)

$$Z_0 = \frac{120\pi}{\sqrt{\epsilon_{eff}} \left(1.393 + \frac{w}{h} + 0.667 \ln \left(\frac{w}{h} + 1.444 \right) \right)}$$

where $\varepsilon_{eff} = \frac{\varepsilon_r + 1}{2} + \frac{\varepsilon_r - 1}{2} \left(1 + 12 \frac{h}{w}\right)^{-0.5}$



Synthesis or design:

1. If the line width is narrow ($w/h < 2$)


$$\frac{w}{h} = \frac{8e^A}{e^{2A} - 2}$$

where $A = \frac{Z_0}{60} \sqrt{\frac{\varepsilon_r + 1}{2}} + \frac{\varepsilon_r - 1}{\varepsilon_r + 1} \left(0.23 + \frac{0.11}{\varepsilon_r} \right)$

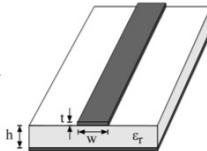2. If the line width is wide ($w/h \geq 2$)

$$\frac{w}{h} = \frac{2}{\pi} \left\{ B - 1 - \ln(2B-1) + \frac{\varepsilon_r - 1}{2\varepsilon_r} [\ln(B-1)] + 0.39 - \frac{0.61}{\varepsilon_r} \right\}$$

$$\text{where } B = \frac{377\pi}{2Z_0\sqrt{\epsilon_r}}$$



80. $S = H$

$$Z = 1.6 - j \frac{2\pi \cdot 58.5 \text{ Hz}}{B_0}$$

$= 1.6 - j 0.428$

$$= j 0.28 - j \frac{2\pi}{w_0}$$

$\Im = 0.28$; $\Re = 0.3$.

$$V = j 0.19 = j \frac{1}{w_0 L}$$

$$L = \frac{50}{2\pi \cdot 58.5 \cdot 1.1}$$

$$L = \frac{50}{4\pi \cdot 9}$$

$$\Rightarrow 20.49 \text{ mH} (\text{!})$$